

problem: What is the inductive reactance of a coil if the current through it is 20 mA and voltage across it is 100V.

Solⁿ: $E_L = I X_L \therefore X_L = \frac{E_L}{I} = \frac{100}{20 \times 10^{-3}} = 5 \text{ k}\Omega$


problem: A capacitor of 50 pF is connected to an ac source of frequency 1 kHz. Calculate its reactance.

Solⁿ: $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 10^3 \times 50 \times 10^{-12}} = \frac{10^7}{\pi} \Omega$

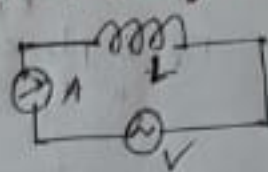problem: In given ckt. applied voltage $V = 50\sqrt{2} \sin(100\pi t)$ volt and ammeter reading is 2A then calculate value of L.


Solⁿ: $E_{\text{rms}} = I_{\text{rms}} X_L$ Reading of ammeter = I_{rms}

$$X_L = \frac{E_{\text{rms}}}{I_{\text{rms}}} = \frac{E_0}{\sqrt{2} I_{\text{rms}}} = \frac{50\sqrt{2}}{\sqrt{2} \cdot 2} = 25 \Omega \Rightarrow L = \frac{X_L}{\omega} = \frac{25}{100\pi} = \frac{1}{4\pi} \text{ H.}$$



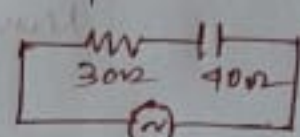problem: Calculate the impedance of the ckt.


Solⁿ: $Z = \sqrt{R^2 + (X_L)^2} = \sqrt{(30)^2 + (40)^2} = \sqrt{2500} = 50 \Omega$



Solⁿ: $Z = X_L - X_C = (50 - 40) \Omega = 10 \Omega$


$I_0 = \frac{E_0}{Z} = \frac{40}{10} = 4 \text{ A}$

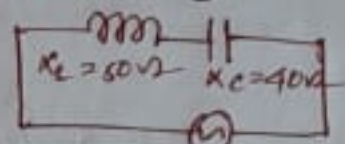$I_{\text{rms}} = \frac{4}{\sqrt{2}} = 2\sqrt{2} \text{ A}$



Solⁿ: $E^2 = E_R^2 + E_L^2 \Rightarrow E_L^2 = E^2 - E_R^2$

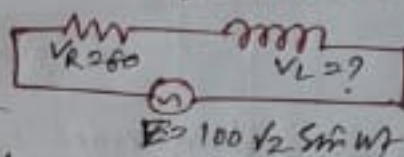
$E_L = \sqrt{E^2 - E_R^2} = \sqrt{100^2 - 60^2} = \sqrt{6400} = 80 \text{ Volt.}$



Solⁿ: $Z = \sqrt{R^2 + X_L^2} = \sqrt{6^2 + 8^2} = 10 \Omega$

$E = I Z \Rightarrow I = \frac{E_0}{Z} = \frac{20}{10} = 2 \text{ A}$

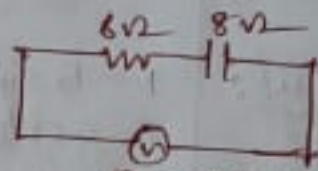$I_{\text{rms}} = \frac{2}{\sqrt{2}} = \sqrt{2} \text{ A.}$



problem: When 10V DC is applied across a coil current through it is 2.5 A, if 10V, 50 Hz AC is applied current reduces to 2A. Calculate reactance of the coil.

Solⁿ: For 10V DC $\therefore E = IR \Rightarrow R = \frac{E}{I} = \frac{10}{2.5} = 4 \Omega$

For 10V AC $\therefore E = I Z \Rightarrow 2 = \frac{E}{Z} = \frac{10}{Z} = 5 \Omega$

$Z = \sqrt{R^2 + X_L^2} = 5 \Rightarrow R^2 + X_L^2 = 25 \Rightarrow X_L^2 = 25 - 4^2 \Rightarrow X_L = 3 \Omega.$


problem:

: COSMIC IN:
FOR KNOWLEDGE

Suman Kumar Bora, A.T.
Physics
7908843766

L-C-R circuit:
Series L-C-R ckt

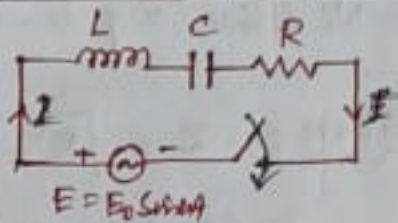$E = E_0 \sin \omega t$
 $E_R = IR, E_L = L \frac{dI}{dt}, E_C = \frac{q}{C}$



By Kirchhoff's law:

$E_R + E_L + E_C = E$

$\therefore IR + L \frac{dI}{dt} + \frac{q}{C} = E_0 \sin \omega t$

Differentiate & rearranging we get \Rightarrow

$\therefore \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = \omega E_0 \cos \omega t$

a. $\therefore \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{I}{C} = \omega E_0 \cos \omega t$ ($\because I = \frac{dq}{dt}$)

After solving this differential equation we get \Rightarrow

$I = \frac{E_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} \sin(\omega t - \phi) = \frac{E_0}{Z} \sin(\omega t - \phi) = I_0 \sin(\omega t - \phi)$

Phase:

E_R is in phase with I $\vec{OP} = E_R$

E_L leads I by 90° $\vec{OQ} = E_L$

E_C lags behind I by 90° $\vec{OS} = E_C$

So E_L & E_C are opposite to each other.

• If $E_L > E_C$ i.e. $\omega L > 1/\omega C$ i.e. $I_0 \omega L > I_0/\omega C$ then

$\vec{OT} = E_L - E_C = \omega L - 1/\omega C$
or $I_0(\omega L - 1/\omega C)$

$\vec{OR} = \vec{E} =$ Resultant of E_R & $(E_L - E_C) =$ applied emf.

$\therefore E = \sqrt{E_R^2 + (E_L - E_C)^2} = I \sqrt{R^2 + (\omega L - 1/\omega C)^2} \Rightarrow I = \frac{E}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} = \frac{E}{Z}$


$Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2} = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$
 $=$ Impedance of the CRT.

$\tan \phi = \frac{(\omega L - 1/\omega C)}{R} = \frac{(\omega L - 1/\omega C)}{R}$

• If $E_L < E_C$ i.e. $\omega L < 1/\omega C$ i.e. $I_0 \omega L < I_0/\omega C$ then


$OU = (1/\omega C - \omega L) = (1/\omega C - \omega L) I_0$

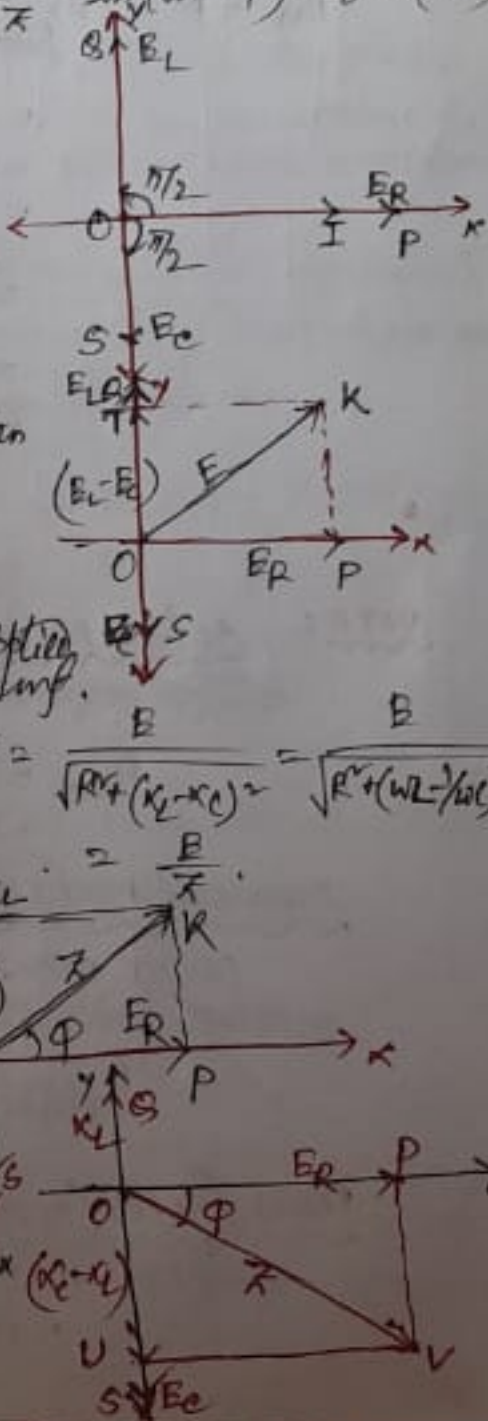$\vec{OV} = \vec{E} = \sqrt{E_R^2 + (E_C - E_L)^2}$
 $= I \sqrt{R^2 + (\omega L - 1/\omega C)^2}$



NOTE: $\omega L > \frac{1}{\omega C}$ then ϕ is +ve i.e. I lags behind by phase or $X_L > X_C$
 $\& \omega L < \frac{1}{\omega C}$ " ϕ is -ve i.e. I leads by phase, or $X_L < X_C$

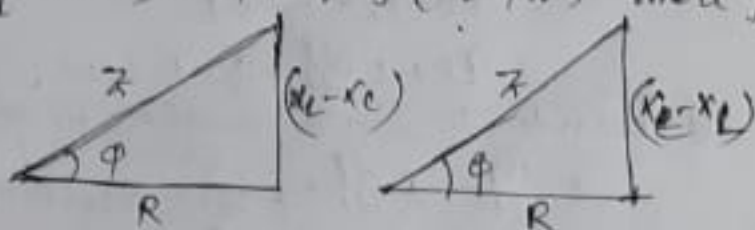Impedance: $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$ = Impedance of the R-C-R circuit.
 In complex quantity: $Z = R + j(\omega L - \frac{1}{\omega C})$ where $j = \sqrt{-1}$.



Dissipative power:

$$P = E I = E_0 \sin \omega t \cdot I_0 \sin(\omega t - \phi)$$

$$= E_0 I_0 (\sin^2 \omega t \cos \phi - \sin \omega t \cos \omega t \sin \phi)$$

$$P_{av} = \bar{P} = \langle P \rangle_{\text{full cycle}} = \frac{1}{T} \int_0^T E_0 I_0 (\sin^2 \omega t \cos \phi - \sin \omega t \cos \omega t \sin \phi) dt$$

$$= \frac{E_0 I_0}{T} \left[\cos \phi \int_0^T \sin^2 \omega t dt - \frac{1}{2} \sin \phi \int_0^T \sin 2\omega t dt \right]$$

$$= \frac{E_0 I_0}{T} (\cos \phi \cdot \frac{T}{2} - \frac{1}{2} \sin \phi \cdot 0) = \frac{E_0 I_0}{2} \cos \phi$$

$$= \frac{E_0}{\sqrt{2}} \frac{I_0}{\sqrt{2}} \cos \phi$$

$$= E_{rms} I_{rms} \cos \phi$$

$$= P_{rms} \cos \phi$$

$$\because \int_0^T \sin^2 \omega t dt = \frac{1}{2} \int_0^T (\cos 2\omega t - 1) dt = \frac{T}{2}$$

$$\because \int_0^T \sin 2\omega t dt = 0$$

$$P_{rms} = E_{rms} I_{rms} = \frac{E_0}{\sqrt{2}} \frac{I_0}{\sqrt{2}}$$

NOTE: Active power or True power (ଅକ୍ଟ/ନିରୀକ୍ଷଣ): କେବଳ ପ୍ରକୃତ ଅକ୍ଟ/ନିରୀକ୍ଷଣ କରାଯାଇଥିବା କାର୍ଯ୍ୟ (ଅକ୍ଟ/ନିରୀକ୍ଷଣ) କରାଯାଇଥାଏ। True or active power of AC.
 $P_{true} = \frac{E_0 I_0}{2} \cos \phi = \langle P \rangle = \bar{P}$

Apparent power or Reactive power (ଅନୁମତ/ଅନୁମତ): ଏହା ପ୍ରକୃତ ଅକ୍ଟ/ନିରୀକ୍ଷଣ କରାଯାଇଥିବା କାର୍ଯ୍ୟ (ଅନୁମତ/ଅନୁମତ) କରାଯାଇଥାଏ।
 $P_{apparent} = P_{rms} = I_{rms} E_{rms} = \frac{I_0}{\sqrt{2}} \cdot \frac{E_0}{\sqrt{2}}$

Power factor (ଅନୁମତ): କେବଳ ପ୍ରକୃତ ଅକ୍ଟ/ନିରୀକ୍ଷଣ କରାଯାଇଥିବା କାର୍ଯ୍ୟ (ଅନୁମତ/ଅନୁମତ) କରାଯାଇଥାଏ।
 $\therefore \text{power factor} = \frac{\text{Average True Power}}{\text{Average Apparent Power}} = \frac{\bar{P}}{P_{rms}} = \cos \phi = \frac{R}{Z}$

• Halfless current (ଅର୍धସାମାନ୍ୟ): ଏହା ଘଟେ ଯେତେବେଳେ $\phi = 90^\circ$ ବା $\phi = 270^\circ$ ହୁଏ, ଯେଉଁଠି $\sin \phi = 1$ ବା $\sin \phi = -1$ ହୁଏ, ତେଣୁ $I_{rms} = \frac{E_{rms}}{Z}$ ହୁଏ।
 ଯଦି $\phi = 90^\circ$ ବା 270° ହୁଏ, ତେଣୁ $\sin \phi = 1$ ବା $\sin \phi = -1$ ହୁଏ, ତେଣୁ $I_{rms} = \frac{E_{rms}}{Z}$ ହୁଏ।
 ଯଦି $\phi = 90^\circ$ ବା 270° ହୁଏ, ତେଣୁ $\sin \phi = 1$ ବା $\sin \phi = -1$ ହୁଏ, ତେଣୁ $I_{rms} = \frac{E_{rms}}{Z}$ ହୁଏ।

• Resonance (ରାଜ୍ୟାମି):

A circuit is said to be resonant when the natural frequency of circuit is equal to frequency of the applied voltage.

For resonance both L and C must present in circuit.

- Series Resonance (କ୍ରମିକ ରାଜ୍ୟାମି)
- Parallel Resonance (ସମାନ୍ୟ ରାଜ୍ୟାମି)

• Series Resonance: In R-C-R series CRT, $X_L = X_C$ then $\phi = 0$.

So impedance Z is minimum which equal to the resistance R. So that the current in the CRT. is maximum means power is maximum. This is called series resonance.

• Series at Resonance:
 $X_L = X_C$
 $E_L = E_C$
 $\phi = 0$ (i.e. E_R & I are in phase)
 Then $Z_{min} = R$ (Impedance minimum)
 $I_{max} = \frac{E_R}{R}$ (Current maximum)
 Power = maximum.

• Resonance frequency: $X_L = X_C \Rightarrow \omega_r L = \frac{1}{\omega_r C} \Rightarrow \omega_r^2 = \frac{1}{LC} \Rightarrow 2\pi f_r = \frac{1}{\sqrt{LC}}$
 $\therefore f_r = \frac{1}{2\pi\sqrt{LC}}$

• Variation of Z with f :

If $f < f_r$ then $X_L < X_C$: $\phi = -ve$ the CRT. nature is capacitive.


At $f = f_r$ then $X_L = X_C$: $\phi = 0$, the CRT. nature is resistive.

If $f > f_r$ then $X_L > X_C$: $\phi = +ve$, the CRT. nature is inductive.

• Variation of I with f : As f increases, Z first decreases then increases.

As f increases I 1st increases then decreases.

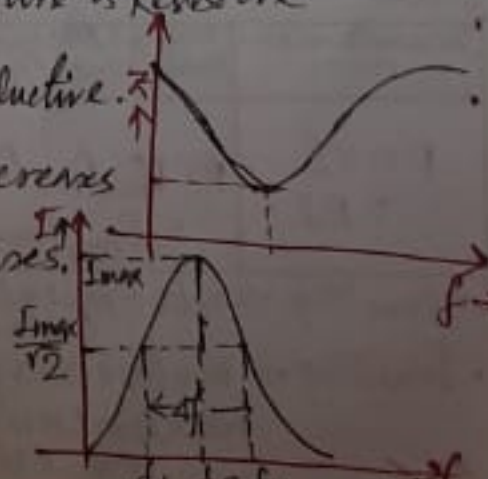• At resonance $Z = \text{minimum}$ so it is called acceptor circuit. It most readily accepts that current out of many currents whose frequency is equal to its natural frequency.



• In radio or TV tuning we receive the desired station by making the frequency of the circuit equal to that of the desired station.

Half power frequency:

The frequency at which power becomes half of its maximum value is called half power frequencies.

• Band width: $\Delta f = f_2 - f_1$

• Quality factor (Q): Q-factor of AC circ. basically gives an idea about stored energy and lost energy.

$$Q = 2\pi \frac{\text{maximum energy stored per cycle}}{\text{maximum energy loss per cycle}}$$

It represents the sharpness of resonance. It is unit less and dimension less quantity.

$$Q = \frac{(X_L)_\omega}{R} = \frac{(X_C)_\omega}{R} = \frac{2\pi f_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{f_0}{\Delta f} = \frac{f_0}{\text{band width}}$$

Magnification:

At resonance

$$E_L = E_C = Q E \quad (E = \text{supply voltage})$$


So at resonance

Magnification factor = Q factor

Sharpness (Q-factor):

• Band width $= 4\omega \Rightarrow \omega_2 - \omega_1 = R/L$ (at $\omega = 2\pi f_0 = 1/\sqrt{LC}$)
 = (at $\omega = 2\pi f_0$)
 width $\Delta \omega$
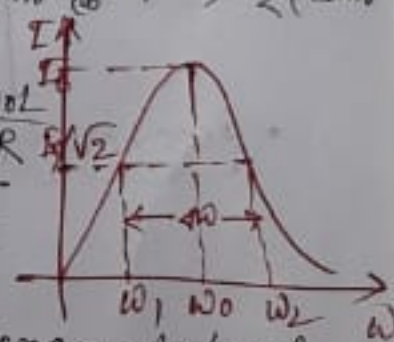
$$Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{\omega_0}{R/L} = \frac{\omega_0 L}{R} = \frac{L}{R} \cdot \frac{1}{\sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$



• If Q is high then resonance is also sharp.


Sharpness \propto Quality factor (Q-factor) \propto Magnification factor.

R decreases \Rightarrow Q increases \Rightarrow Sharpness increases

NOTE

Instantaneous power	Average/Actual/Disippative power/Power loss	Virtual/Apparent/Prms power	Peak power
$P = VI = EI$	$P = I_{rms} I_{rms} \cos \phi = E_{rms} I_{rms} \cos \phi$	$P = V_{rms} I_{rms} = E_{rms} I_{rms}$	$P = V_0 I_0 = E_0 I_0$

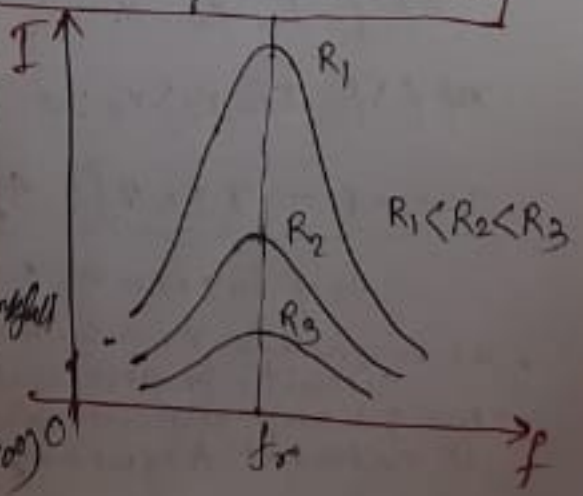- $I_{rms} \cos \phi \Rightarrow$ active part of current or wattfull current or workfull current. It is in phase with voltage.
- $I_{rms} \sin \phi \Rightarrow$ inactive part of current, wattless current, workless current. It is in quadrature (90°) with voltage.



Problem: What is the inductive reactance of a coil if the current through it is 20 mA and voltage across it is 100 volt.


Solⁿ: $E_L = I X_L \therefore X_L = \frac{E_L}{I} = \frac{100}{20 \times 10^{-3}} = 5k\Omega$

Problem: A capacitor of 50 pF is connected to an ac source of frequency 1 kHz. Calculate its reactance?

Solⁿ: $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 10^3 \times 50 \times 10^{-12}} = \frac{10^7}{\pi} \Omega$

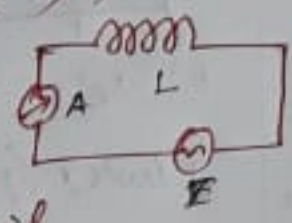
Problem: In the circ. applied voltage $E = 50\sqrt{2} \sin(100\pi t)$ Volt and ammeter reading is 2A then calculate value of L?

Solⁿ: $E_{rms} = I_{rms} X_L$
Solve before.



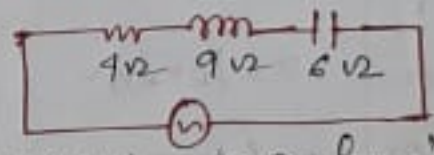Problem: Find the impedance of given circuit.


Solⁿ: $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{4^2 + (9-6)^2}$
 $= \sqrt{4^2 + 3^2} = \sqrt{25} = 5\Omega$



($\because X_L > X_C \therefore$ Inductive)

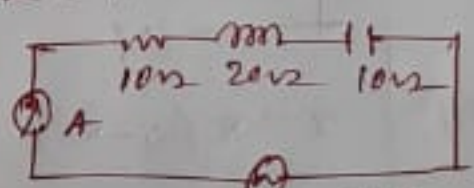Problem: Find out the reading of ac ammeter and also calculate the potential difference of given L-C-R circ.

Solⁿ: $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{10^2 + (20-10)^2}$
 $= 10\sqrt{2} \Omega$



$E = 100 \sin(100\pi t)$ Volt

$I_0 = \frac{E_0}{Z} = \frac{100}{10\sqrt{2}} = \frac{10}{\sqrt{2}} A$

$I_{rms} = \frac{10}{\sqrt{2} \cdot \sqrt{2}} = 5 A$ (Ammeter reads RMS value).


$E_R = 5 \times 10 = 50 V$
 $E_C = 5 \times 10 = 50 V$

Problem: In LCR circ. with an ac source $R = 300\Omega$, $C = 20\mu F$, $L = 1.0 H$, $E_{rms} = 50V$ and $f = 50/\pi$ Hz. Find rms value of ac?

Solⁿ: $I_{rms} = \frac{E_{rms}}{Z} = \frac{E_{rms}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{50}{\sqrt{300^2 + [2.5 \times \frac{50}{\pi} \times 1 - \frac{1}{20 \times 10^{-6} \times 25 \times 50/\pi]^2}}$
 $= \frac{50}{\sqrt{(300)^2 + [100 - \frac{10^3}{2}]^2}} = \frac{50}{100\sqrt{9+16}} = \frac{1}{10} = 0.1 A$

Problem: For what frequency the voltage across the resistance R will be maximum.

Solⁿ: It happens at resonance

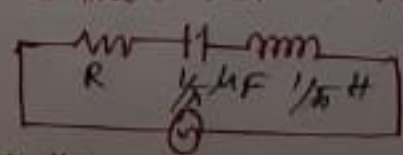


$f = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{\frac{1}{\pi} \times 10^{-6} \times \frac{1}{\pi}}} = 500 Hz$

problem: In series L-C-R circ. find V_L ?

soln: $\omega L = \frac{1}{\omega C}$ at resonance.

$$C = \frac{1}{\omega^2 L} = \frac{1}{(2\pi \times 60)^2 \times 10^{-3}} = 175.4 \mu F$$
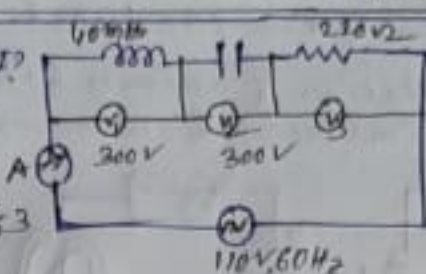
$$\therefore V_L = V_R \Rightarrow V_L = 110V \text{ and } I = \frac{V}{R} = \frac{110}{20} = 0.5A$$



problem: Radio receiver receives a message at 300m band, if the available inductance is 1mH, then calculate required capacitance.

soln: Radio receives EM waves ($V_{EM} = 3 \times 10^8 \text{ m/s} = c$)

$$c = \lambda \nu \Rightarrow \lambda = \frac{3 \times 10^8}{300} = 10^6 \text{ Hz.}$$

$$f = \frac{1}{2\pi \sqrt{LC}} = 1 \times 10^6 \Rightarrow C = \frac{1}{4\pi^2 \times 10^{-3} \times 10^{12}} = 25 \text{ pF.}$$

choke coil: In DC circ. current is reduced with the help of a resistance. Loss of electrical energy is produced in form of heat in the resistor. In AC circ. it is done by choke coil.

choke coil is a copper coil acts as an simple inductor is used to reduced current in ac circ. without much loss of energy.

principle: The working of a choke is based on the working of an inductor. When ac flows through it then current lags behind the emf by phase $\frac{\pi}{2}$ radian.

working: Chk. of choke coil is a series L-R circ.

If resistance of choke coil = r (very small)

$$\text{Then current } I = \frac{E}{Z}; Z = \sqrt{(R+r)^2 + (\omega L)^2}$$


$R \rightarrow$ resistance of the electrical appliance.

$$P_{av} = E_{eff} I_{eff} \cos \phi = E_{eff} I_{eff} \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \quad (\text{neglecting } r)$$

$$\text{Power loss in the choke } P_{av} = E_{rms} I_{rms} \cos \phi \rightarrow 0.$$

$$\therefore \cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \approx \frac{R}{\omega L} \rightarrow 0 \quad (\text{as } L \text{ is very large})$$

$R \ll \omega L$

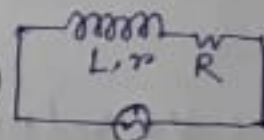

problem: If power factor of a R-L circ. is $\frac{1}{2}$ when applied voltage is $V = 100 \sin 100\pi t$ volt and resistance of circ. is $200\sqrt{2}$ then calculate the inductance of the circ.

$$\text{soln: } \cos \phi = R/Z \Rightarrow \frac{1}{2} = R/Z \Rightarrow Z = 2R \Rightarrow \sqrt{R^2 + \omega^2 L^2} = 2R$$

$$\omega L = \sqrt{3} R = \omega L \Rightarrow L = \frac{\sqrt{3} R}{\omega} = \frac{\sqrt{3} \times 200}{100\pi} = \frac{2\sqrt{3}}{\pi} \text{ H}$$


problem: A circ. consisting of an inductance and a resistance joined to a 200 volt supply (AC). It draws a current of 10 A. If the power consumed the circ. is 1500 Watt. Calculate the Wattless current.

$$\text{soln: } \text{Apparent power} = 200 \times 10 = 2000 \text{ W}$$

$$\text{power factor } \cos \phi = \frac{\text{True power}}{\text{Apparent power}} = \frac{1500}{2000} = \frac{3}{4}$$

$$\text{Wattless current } I_{\text{wattless}} = I_{\text{rms}} \sin \phi = 10 \sqrt{1 - (3/4)^2} = \frac{10\sqrt{7}}{4} \text{ A}$$

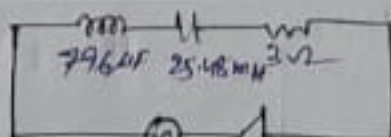Problem: Find X_L , X_C , Z , ϕ , I_{rms} , P_{av} & power factor?



Solⁿ: $E_0 = 230V$, $f = 50\text{ Hz}$, $R = 3\Omega$,
 $L = 25.48\text{ mH}$, $C = 796\text{ }\mu\text{F} = 796 \times 10^{-6}\text{ F}$
 $= 25.48 \times 10^{-3}\text{ H}$.

$$\therefore X_L = 2\pi fL = 2 \times 3.14 \times 50 \times 25.48 \times 10^{-3} = 8\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 50 \times 796 \times 10^{-6}} = 4\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{3^2 + (8-4)^2} = 5\Omega$$

$$\tan\phi = \frac{X_L - X_C}{R} = \frac{8-4}{3} = \frac{4}{3} \Rightarrow \phi = \tan^{-1}\left(\frac{4}{3}\right) = 53.1^\circ$$

$$I_{rms} = \frac{I_0}{\sqrt{2}} = \frac{E_0}{\sqrt{2}Z} = \frac{1}{1.414} \times \frac{230}{5} = 40\text{ A}$$

$$P_{av} = I_{rms}^2 R = 40^2 \times 3 = 4800\text{ W}$$

$$\text{Power factor} = \cos\phi = \cos 53.1^\circ = 0.6 = \frac{R}{Z} = \frac{3}{5} = 0.6$$

$$Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{3} \sqrt{\frac{25.48 \times 10^{-3}}{796 \times 10^{-6}}} = \frac{1}{3} \sqrt{32101} = \frac{5.67}{3} = 1.89$$

Transformer:



A transformer is a electrical device, based on the principle of mutual inductance, used for converting large alternating current at low voltage into small current at high voltage and vice versa.

Transformer two types

- Step up: The transformer which convert low voltages into higher ones called step up transformer
- Step down: The transformer which convert high voltages into lower ones called step down transformer.


Step up

Step down

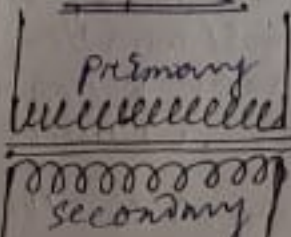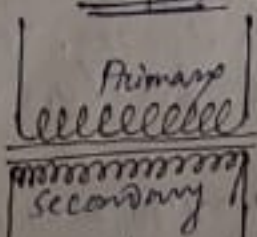

(Coil type transformer)
(Shell type transformer)

Working formula:

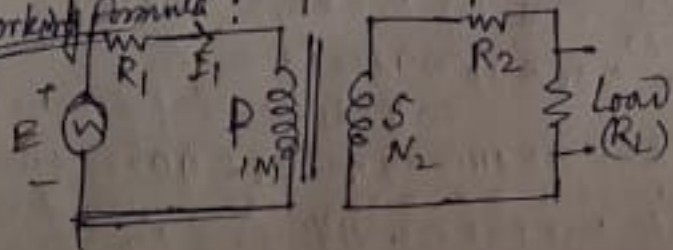

$N_1 \rightarrow$ no. of turns in the primary coil

$N_2 \rightarrow$ " " " " " Secondary "

Induced emf in the primary coil $E_1 = -N_1 \frac{d\phi}{dt}$

" " " " " Secondary coil $E_2 = -N_2 \frac{d\phi}{dt}$

$$\therefore \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$E \rightarrow$ applied emf in the primary. But by Lenz's law self induced emf E_1 opposes E in the primary coil.

\therefore Resultant emf in the primary = $E - E_1$

$$\therefore E - E_1 = R_1 I_1 \text{ But } R_1 \text{ is very small, so } E - E_1 = 0 \text{ i.e. } E = E_1$$

$$\therefore K = \frac{E_2}{E_1} = \frac{\text{output emf}}{\text{input emf}} = \frac{N_2}{N_1} = \text{transformer ratio.}$$

For step up transformer: $N_2 > N_1$ i.e. $N_2/N_1 > 1$ i.e. $E_2 > E_1$ i.e. output voltage is greater than input voltage.

step down $N_2 < N_1$ i.e. $N_2/N_1 < 1$ i.e. $E_2 < E_1$ i.e. output voltage is less than input voltage.

Currents in primary & secondary coils:

Let transformer to be ideal so that there are no energy loss.

Input power = output power i.e. $E_1 I_1 = E_2 I_2$

$$\therefore I_1/I_2 = E_2/E_1 \text{ i.e. } \boxed{I_1/E_2 = E_2/E_1 = N_2/N_1}$$

Efficiency of a transformer:

$$\eta = \frac{\text{output power}}{\text{input power}} \times 100\%$$

It be 90 to 99% for a transformer.

Use: i) In radio, telephones, loud speakers etc.

ii) tv, refrigerators, air conditioners, computers etc used voltage regulator.

iii) stabilised power supplies.

iv) step up & step down transformer used in any electrical appliances.

v) In power station.

Energy losses in transformers: 1) Copper loss

2) Eddy current loss, 3) Hysteresis loss, 4) Flux leakage

5) Humming loss etc.

Problem: The primary coil of an ideal step up transformer has 100 turns and the transformation ratio is also 100. The input voltage & the power are 220V & 1100W respectively. Calculate.

i) N_2 , ii) I_1 , iii) E_2 , iv) I_2 , v) Power?

Solⁿ: $N_1 = 100$ 1) $k = \frac{N_2}{N_1} = 100 \Rightarrow N_2 = 100, N_1 = 100 \times 100 = 10,000$

$$E_1 = 220V$$

$$P_1 = 1100W$$

$$ii) I_1 = P_1/E_1 = \frac{1100}{220} = 5A \quad iii) E_2 = kE_1 = 100 \times 220 = 22000V$$

$$iv) I_2 = I_1/k = 5/100 = 0.05A \quad v) \text{ For ideal transformer}$$

$$\text{output power} = \text{input power} = 1100W$$

Problem: A transformer efficiency 100% has 200 primary turns & 40000 turns in secondary. It is connected to 220V ac mains & secondary feeds to a resistance 100k Ω . Calculate output pot. difference per turn and the power delivered to the load?

Solⁿ: $\eta = 100\%$, $N_1 = 200$, $N_2 = 40,000$, $E_1 = 220V$, $R_2 = 100k\Omega = 10^5 \Omega$


$$k = E_2/E_1 = N_2/N_1 \Rightarrow E_2 = \frac{N_2}{N_1} E_1 = \frac{40000}{200} \times 220 = 44000V$$

$$\text{output pd/turn} = \frac{E_2}{N_2} = \frac{44000}{40000} = 1.1V \quad \text{Power delivered to load} = \frac{E_2^2}{R} = \frac{(44000)^2}{10^5} = 19360W = 19.36kW$$

Electromagnetic wave (ଦେଖିବା ପାଇଁ):

ପରିବର୍ତ୍ତନୀୟ ବିଦ୍ୟୁତ୍ କ୍ଷେତ୍ର ପରିବର୍ତ୍ତନୀୟ ଚୁମ୍ବକ କ୍ଷେତ୍ର ସୃଷ୍ଟି କରେ ଏବଂ ବିପରୀତ ଭାବରେ ଚୁମ୍ବକ କ୍ଷେତ୍ରର ପରିବର୍ତ୍ତନ ବିଦ୍ୟୁତ୍ କ୍ଷେତ୍ର ସୃଷ୍ଟି କରେ। ଏହି ଦୁଇ କ୍ଷେତ୍ର ମଧ୍ୟରେ ଯେଉଁ ପାରସ୍ପରିକ କ୍ରିୟା ଘଟେ, ତାହାକୁ ବିଦ୍ୟୁତ୍ ଚୁମ୍ବକ ତରଙ୍ଗ କୁହାଯାଏ।

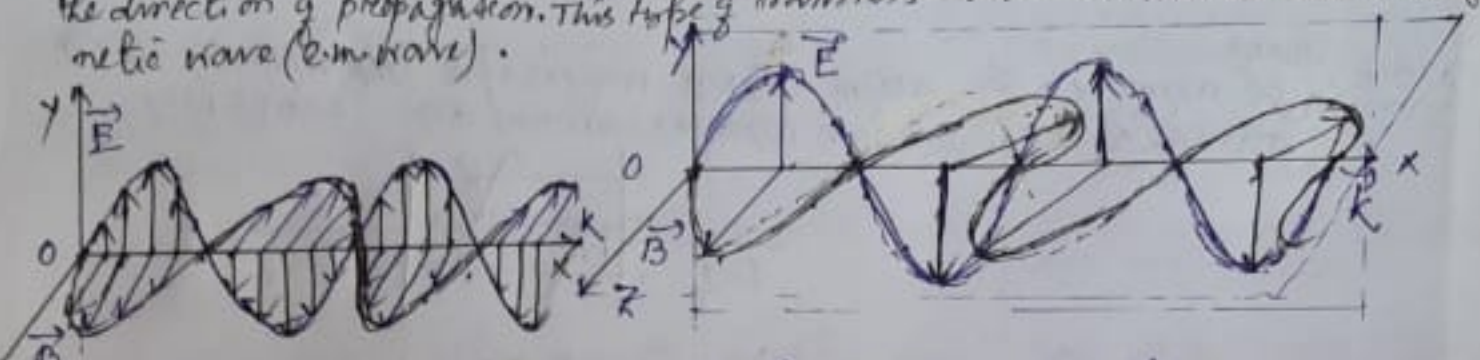A changing electric field produces a changing magnetic field and vice-versa which are acting at right angles to each other as well as at right angles to the direction of propagation. This type of transverse wave known as electromagnetic wave (em-wave).



$$\vec{E} = \vec{E}_0 \sin \omega(t - z/c) = \vec{E}_0 \sin(\omega t - kz)$$

$$\vec{B} = \vec{B}_0 \sin \omega(t - z/c) = \vec{B}_0 \sin(\omega t - kz)$$

$E_0, B_0 \rightarrow$ ବିଦ୍ୟୁତ୍ ଓ ଚୁମ୍ବକ କ୍ଷେତ୍ରର ଅମ୍ଳିତ ମାନ
 $\omega, k \rightarrow$ କୋଣିକ କମ୍ପାଂସ ଓ କୋଣିକ ସଂଖ୍ୟା

Displacement Current (ସଂକଳିତ ବିଦ୍ୟୁତ୍):

କ୍ୟାପାସିଟରର ପ୍ଲେଟ୍ ମଧ୍ୟରେ ବିଦ୍ୟୁତ୍ କ୍ଷେତ୍ରର ପରିବର୍ତ୍ତନ ହେତୁ ଏହାକୁ ସଂକଳିତ ବିଦ୍ୟୁତ୍ କୁହାଯାଏ। ଏହା ବିଦ୍ୟୁତ୍ ବିଦ୍ୟୁତ୍ କ୍ଷେତ୍ରର ପରିବର୍ତ୍ତନ ଯୋଗୁଁ ସୃଷ୍ଟି ହୁଏ।

It is the current due to changing electric field between the plate of the capacitor and denoted as I_d .


The current due to the flow of charges in a conductor and is denoted as I_c known as the conduction current.

ସମଗ୍ର ବିଦ୍ୟୁତ୍ ବିଦ୍ୟୁତ୍ $I = I_c + I_d$

Concept of I_d :

ଯଦି ଏକ କ୍ୟାପାସିଟରର ପ୍ଲେଟ୍ ମଧ୍ୟରେ Q ଚାର୍ଜ ରଖାଯାଏ, ତେବେ ଏହା ଏକ ବିଦ୍ୟୁତ୍ କ୍ଷେତ୍ର ସୃଷ୍ଟି କରେ। ଏହି କ୍ଷେତ୍ରର ପରିବର୍ତ୍ତନ ଯୋଗୁଁ ସଂକଳିତ ବିଦ୍ୟୁତ୍ ସୃଷ୍ଟି ହୁଏ। ଏହାକୁ ସଂକଳିତ ବିଦ୍ୟୁତ୍ କୁହାଯାଏ। ଏହା ବିଦ୍ୟୁତ୍ ବିଦ୍ୟୁତ୍ କ୍ଷେତ୍ରର ପରିବର୍ତ୍ତନ ଯୋଗୁଁ ସୃଷ୍ଟି ହୁଏ। ଏହାକୁ ସଂକଳିତ ବିଦ୍ୟୁତ୍ କୁହାଯାଏ। ଏହା ବିଦ୍ୟୁତ୍ ବିଦ୍ୟୁତ୍ କ୍ଷେତ୍ରର ପରିବର୍ତ୍ତନ ଯୋଗୁଁ ସୃଷ୍ଟି ହୁଏ। ଏହାକୁ ସଂକଳିତ ବିଦ୍ୟୁତ୍ କୁହାଯାଏ।

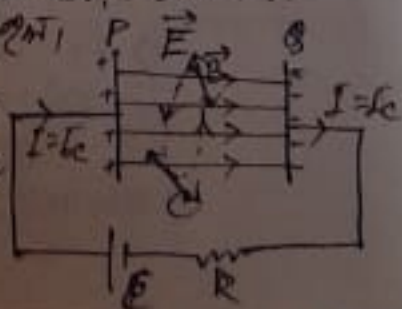Electric field: $E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$; $A \rightarrow$ Area of the plate.
 In time dt charge on the plate of the capacitor increases by dQ
 \therefore change in electric field $dE = \frac{dQ}{\epsilon_0 A} = \frac{I dt}{\epsilon_0 A}$



$$\therefore \frac{dE}{dt} = \frac{I}{\epsilon_0 A} \Rightarrow I = \epsilon_0 A \frac{dE}{dt} = \epsilon_0 \frac{d}{dt}(AE) = \epsilon_0 \frac{d\Phi_E}{dt} \quad (\because \Phi_E = AE)$$


$$\therefore \boxed{I_d = \epsilon_0 \frac{d\Phi_E}{dt}}$$

Maxwell's circuital law (2nd)

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 (I_c + I_d) = \mu_0 (I_c + \epsilon_0 \frac{d\Phi_E}{dt})$$

This is known as Maxwell-Ampere's circuital law.

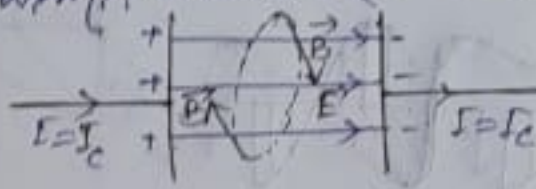NOTE: μ_0 is the permeability of free space and ϵ_0 is the permittivity of free space.



• The speed of light in vacuum is given by -

$$c = \frac{1}{\sqrt{\mu_0 \epsilon_0}} \quad ; \quad \mu_0 \rightarrow \text{permeability of free space} = 4\pi \times 10^{-7} \text{ N/A}^2$$

$$\epsilon_0 \rightarrow \text{permittivity of free space} = 8.854 \times 10^{-12} \text{ C}^2/\text{Nm}^2$$

$$\therefore c = \frac{1}{\sqrt{4\pi \times 10^{-7} \times 8.854 \times 10^{-12}}} = 3 \times 10^8 \text{ m/sec.}$$

• The speed of light in a medium is given by $v = \frac{1}{\sqrt{\mu_0 \mu_r \epsilon_0 \epsilon_r}}$

Properties of e.m. wave:

- 1) E.M. wave travels in straight line.
- 2) It is produced by accelerated charges.
- 3) E.M. wave travels with speed of light in vacuum.
- 4) It is a transverse wave.
- 5) Its speed is $c = \frac{1}{\sqrt{\mu_0 \epsilon_0}} = 3 \times 10^8 \text{ m/sec}$.
- 6) It consists of electric field E and magnetic field B.
- 7) The electric field and magnetic field are perpendicular to each other and to the direction of propagation.
- 8) The ratio of electric field to magnetic field is $E/B = c$.
- 9) It is a transverse wave and it consists of electric and magnetic fields.
- 10) Maxwell's 3rd and 4th e.m. wave equations are:

$$\frac{\partial E}{\partial t} = \mu_0 \epsilon_0 \frac{\partial B}{\partial t}$$

$$\frac{\partial B}{\partial t} = \mu_0 \epsilon_0 \frac{\partial E}{\partial t}$$

- $U_{av} = \frac{1}{2} \epsilon_0 E_0^2 + \frac{B_0^2}{4\mu_0} = \frac{1}{2} \epsilon_0 E_0^2 + \frac{E_0^2}{4\mu_0} \mu_0 \epsilon_0 = \frac{1}{2} \epsilon_0 E_0^2 + \frac{1}{2} \epsilon_0 E_0^2$
 $= \epsilon_0 E_0^2 \quad (\because c = \frac{E_0}{B_0} \text{ and } c = \frac{1}{\sqrt{\mu_0 \epsilon_0}})$
- $U_{av} = \frac{1}{2} \epsilon_0 E_0^2 + \frac{B_0^2}{4\mu_0} = \frac{1}{2} \epsilon_0 \left(\frac{B_0^2}{\mu_0 \epsilon_0} \right) + \frac{B_0^2}{4\mu_0} = \frac{B_0^2}{2\mu_0}$
- $\langle U_E \rangle = \langle U_B \rangle = \frac{1}{2} \epsilon_0 E_0^2 = \frac{1}{2} \epsilon_0 B_0^2 \cdot \frac{1}{\mu_0 \epsilon_0} = \frac{B_0^2}{2\mu_0}$

• Poynting vector (\vec{P} or \vec{S}):

এই ভেক্টরটি নির্দেশ করে যেখানে কোন বিন্দুতে কোন কোন দিকে (যে কোন দিকে) কোন কোন ক্ষেত্রের শক্তি প্রবাহিত হচ্ছে। (কোন দিকে)।
 এটি (কোন) দিকে শক্তি প্রবাহিত হচ্ছে। (Intensity) এর সূত্র

$\vec{S} = \frac{1}{\mu_0} (\vec{E} \times \vec{B})$. Unit: Watt/m^2 in S.I.

The energy crossing per unit area per unit time perpendicular to the direction of propagation is called the intensity of a wave.
 \therefore Intensity of e.m. wave is $U = \text{var}(cA) \Rightarrow I = \frac{U}{A \Delta t} = U_{av}$

$I = |\vec{S}| = \frac{1}{\mu_0} |\vec{E} \times \vec{B}| = \frac{EB}{\mu_0}$ (as $E \perp B$)
 $= \frac{1}{\mu_0} \cdot \frac{E_0}{\sqrt{2}} \cdot \frac{B_0}{\sqrt{2}} = \frac{E_0 B_0}{2\mu_0}$

NOTE: $I = \frac{1}{2} \frac{E_0 B_0}{\mu_0} = \frac{1}{2} \epsilon_0 E_0^2 c = \frac{1}{2} \frac{B_0^2}{\mu_0} c$

• Momentum and pressure of e.m. wave:

কোন বিন্দুতে কোন কোন দিকে শক্তি প্রবাহিত হচ্ছে, তাই শক্তির
 প্রবাহের দিক এবং তার মাত্রা। এই প্রবাহের দিকের পরিমাপকে (Radiation) pressure
 শক্তির প্রবাহের দিকের পরিমাপকে $P = \frac{U}{c}$ (Radiation pressure)

• শক্তি প্রবাহের দিকের পরিমাপ, $P = \frac{2U}{c}$

• শক্তি প্রবাহের পরিমাপ A এর t সময়ের মধ্যে শক্তির পরিমাণ
 $U = I A t$; $I \rightarrow$ Intensity of e.m. wave.

\therefore শক্তির পরিমাণের পরিমাপ $F = \frac{P}{A} = \frac{U}{A t} = \frac{I A t}{A t} = \frac{I A t}{A t}$

\therefore Radiation pressure (Radiation pressure) $P = \frac{F}{A} = \frac{I A t}{A t} = \frac{I A t}{A t} = \frac{I A t}{A t}$

• শক্তি প্রবাহের পরিমাপ $P = \frac{2I}{c}$

Ex- Radiation pressure এর মান $7 \times 10^{-6} \text{ N/m}^2$
 এর মান 0.17 N/m^2 এর মান 0.17 N/m^2

Electromagnetic spectrum:
 The electromagnetic spectrum is the range of all possible frequencies of electromagnetic radiation. It includes radio waves, microwaves, infrared, visible light, ultraviolet, X-rays, and gamma rays.

Wavelength (m)	Frequency (Hz)	Energy (J)	Characteristics
$10^3 \sim 10^4$	$3 \times 10^9 \sim 3 \times 10^{10}$	$6 \times 10^{-18} \sim 6 \times 10^{-17}$	Radio waves, used for communication.
$10^{-11} \sim 10^{-8}$	$10^{16} \sim 3 \times 10^{19}$	$10^{-11} \sim 3 \times 10^{-8}$	X-rays, used in medicine.
$10^{-7} \sim 4 \times 10^{-7}$	$7.5 \times 10^{14} \sim 3 \times 10^{16}$	$3 \times 10^{-19} \sim 4 \times 10^{-17}$	Ultraviolet rays, causes skin cancer.
$4 \times 10^{-7} \sim 7.5 \times 10^{-7}$	$4 \times 10^{14} \sim 7.5 \times 10^{14}$	$4 \times 10^{-19} \sim 8 \times 10^{-19}$	Visible light, what we see.
$10^{-3} \sim 10^{-1}$	$10^{11} \sim 4 \times 10^{14}$	$8 \times 10^{-7} \sim 3 \times 10^{-3}$	Infrared rays, used in remote controls.
$3 \times 10^{-7} \sim 10^{-12}$	$3 \times 10^7 \sim 10^{12}$	$3 \times 10^{-6} \sim 0.1$	Microwaves, used in cooking.
$10^3 \sim 10^4$	$3 \times 10^9 \sim 3 \times 10^{10}$	$6 \times 10^{-18} \sim 6 \times 10^{-17}$	Radio waves, used for communication.

- AM (Amplitude Modulation) frequency range $530 \text{ kHz} \sim 1710 \text{ kHz}$
- FM (Frequency Modulation) frequency range $88 \text{ MHz} \sim 108 \text{ MHz}$
- TV 10 $\rightarrow 54 \text{ MHz} \sim 890 \text{ MHz}$
- Snake \rightarrow Infrared ray
- Insects \rightarrow Ultraviolet ray

Energy density of EM wave:

The energy density of an electromagnetic wave is the energy per unit volume.

$$u_E = \frac{1}{2} \epsilon_0 E^2 \quad \text{and} \quad u_B = \frac{1}{2\mu_0} B^2$$

$$\therefore \text{Total energy density } u = u_E + u_B = \frac{1}{2} \epsilon_0 E^2 + \frac{1}{2\mu_0} B^2$$

$$= \frac{1}{2} \epsilon_0 \{ E_0^2 \sin^2(\omega t - kx) \} + \frac{1}{2\mu_0} \{ B_0^2 \sin^2(\omega t - kx) \}$$

$$\therefore \text{Average energy density } u_{av} = \langle u \rangle = \bar{u}$$

$$= \frac{1}{2} \epsilon_0 E_0^2 \langle \sin^2(\omega t - kx) \rangle + \frac{1}{2\mu_0} \langle B_0^2 \sin^2(\omega t - kx) \rangle$$

$$= \frac{1}{2} \epsilon_0 E_0^2 \cdot \frac{1}{2} + \frac{1}{2\mu_0} \cdot \frac{1}{2} = \frac{1}{4} \epsilon_0 E_0^2 + \frac{1}{4\mu_0} B_0^2$$

problem: Given electric field $E_x = 0$,
 $E_y = 0.5 \cos [2\pi \times 10^8 (t - x/c)]$ and $E_z = 0$.

- a) E.M. wave can also propagate along x-axis,
 b) find ω of e.m. wave
 c) find the eqn of B of this e.m. wave?

Soln:

- a) $E_y = 0.5 \cos [2\pi \times 10^8 (t - x/c)]$ means the wave propagate along +ve x-direction.
 b) compare this wave with $E_y = E_0 \cos \omega (t - x/c)$ then we get
 $\omega = 2\pi \times 10^8 = 2\pi \times 10^8 \Rightarrow n = 10^8 \text{ Hz}$
 $\therefore \lambda = \frac{c}{n} = \frac{3 \times 10^8 \text{ m/s}}{10^8 \text{ Hz}} = 3 \text{ m.}$

c) As E_x & $E_z = 0$ so B_x & $B_y = 0$.

As wave towards x-axis
 \rightarrow E-field along y-axis

so B is in z direction

$$\therefore B_z = B_0 \cos [2\pi \times 10^8 (t - x/c)] = \frac{E_0}{c} \cos [2\pi \times 10^8 (t - x/c)]$$

$$= \frac{0.5}{3 \times 10^8} \cos [2\pi \times 10^8 (t - x/c)]$$

problem: Given e.m. wave as eqn $E = 20 \sin \omega (t - x/c)$ V/m, find intensity of the wave and r.m.s value of electric field?

Soln:

$$E = 20 \sin \omega (t - x/c) \text{ V/m}$$

$$E_0 = 20 \text{ V/m. } I = \frac{1}{2} \epsilon_0 E_0^2 c = \frac{1}{2} \times 8.85 \times 10^{-12} \times 3 \times 10^8 \times 400 = 0.53 \text{ W/m}^2$$

$$E_{\text{r.m.s}} = \frac{E_0}{\sqrt{2}} = \frac{20}{\sqrt{2}} = 10\sqrt{2} = 14.14 \text{ V/m}$$

problem: Given magnetic e.m. wave $B_y = 2 \times 10^{-7} \sin (0.5 \times 10^3 x + 1.5 \times 10^{11} t)$ T

- a) Find the n & λ of the wave.
 b) Find Electric field wave eqn?

Soln:

$$B_y = B_0 \sin [2\pi (\frac{x}{\lambda} + \frac{t}{T})] \text{ Comparing we get}$$

$$2\pi \frac{1}{\lambda} = 0.5 \times 10^3 \Rightarrow \lambda = \frac{2\pi}{0.5 \times 10^3} \text{ m} = 1.26 \text{ cm.}$$

$$2\pi \frac{1}{T} = \frac{1.5 \times 10^{11}}{2\pi} = 23.9 \text{ GHz.}$$

$$B_0 = 2 \times 10^{-7} \text{ T} \Rightarrow E_0 = B_0 c = 2 \times 10^{-7} \times 3 \times 10^8 \text{ V/m} = 60 \text{ V/m.}$$

$$E_x = 60 \sin (0.5 \times 10^3 x + 1.5 \times 10^{11} t) \text{ V/m.}$$

Problem: एक समतल/Plane e.m. wave का E_0 का 2 V/m है, B_0 का 2 T है। $\langle u \rangle$ का मान ज्ञात करें।

Sol: $\langle u \rangle = \frac{1}{4} \frac{B_0^2}{\mu_0} = \frac{1}{4} \frac{E_0^2}{\mu_0 c^2} = \frac{1}{4} E_0 E_0^2 \left(\because B_0 = \frac{E_0}{c} \right) \left(c = \frac{1}{\sqrt{\mu_0 \epsilon_0}} \right)$
 $= \frac{1}{4} \times 8.854 \times 10^{-12} \times 2^2 = 8.854 \times 10^{-12} \text{ J/m}^3$

Problem: एक समतल/Plane e.m. wave का 10 W/m^2 का $\langle u \rangle$ है। 10 m की दूरी पर 10 m^2 का क्षेत्रफल है। $\langle u \rangle$ का मान ज्ञात करें।

Sol: $\phi = 10 \text{ W/m}^2$
 $A = 10 \text{ m}^2$
 $t = 10 \text{ s} = 600 \text{ sec}$
 Total energy $\phi A t = 10 \times 10 \times 600 = 3 \text{ J}$
 $\therefore p = \frac{3 \text{ J}}{3 \times 10^8 \text{ m/s}} = 10^{-8} \text{ kg m/sec}$
 $F = \frac{p}{t} = \frac{10^{-8}}{600} = 1.6 \times 10^{-11} \text{ N}$

\therefore Force in 10 m is $F = \frac{2p}{t} = \frac{2 \times 10^{-8}}{600} = 3.3 \times 10^{-11} \text{ N}$.

Problem: एक e.m. wave का frequency $2 \times 10^{10} \text{ Hz}$, Amplitude 48 V/m है। λ , Amplitude of magnetic field and average energy density ज्ञात करें।

Sol: $\nu = 2 \times 10^{10} \text{ Hz}$
 $E_0 = 48 \text{ V/m}$
 $\lambda = c/\nu = \frac{3 \times 10^8}{2 \times 10^{10}} = 1.5 \times 10^{-2} \text{ m}$
 $c = E_0/B_0 \Rightarrow B_0 = E_0/c = \frac{48}{3 \times 10^8} = 1.6 \times 10^{-7} \text{ T}$
 $u = \frac{1}{2} \epsilon_0 E_0^2 = \frac{1}{2} \times 8.85 \times 10^{-12} \times (48)^2 = 10^{-8} \text{ J/m}^3$

Problem: 25 MHz का एक समतल/Plane e.m. wave का $E = 6.3 \text{ V/m}$ है। B का मान ज्ञात करें।

Sol: $B = E/c = \frac{6.3}{3 \times 10^8} \text{ T} = 2.1 \times 10^{-8} \text{ T}$
 \vec{E} along y-axis & wave along x-axis.
 $\therefore \vec{B}$ is z-axis.

Problem: Find the amplitude of electric field in a parallel beam of light of intensity 2 W/m^2 .

Sol: $I = u_{av} c = \frac{1}{2} \epsilon_0 B_0^2 c \Rightarrow E_0 = \sqrt{\frac{2I}{\epsilon_0 c}} = \sqrt{\frac{2 \times 2.0 \text{ W/m}^2}{8.85 \times 10^{-12} \text{ N} \cdot \text{m}^2/\text{C}^2 \times 3 \times 10^8 \text{ m/s}}} = 38.8 \text{ N/C}$

Problem: 60 cm का एक laser beam 4 mW का 10 m^2 का क्षेत्रफल है। 10 m की दूरी पर 10 m^2 का क्षेत्रफल है। $\langle u \rangle$ का मान ज्ञात करें।

Sol: Time taken $t = \frac{60 \text{ cm}}{c} = 2 \times 10^{-9} \text{ sec}$
 $\therefore U = (4 \text{ mW}) t = 4 \text{ mW} \times 2 \times 10^{-9} \text{ sec} = 8 \times 10^{-12} \text{ J}$